

1. ELECTRICAL CAPACITANCE — FUNDAMENTALS

DEFINITION + BASIC RELATIONSHIPS

When an electric charge Q is supplied to an isolated conductor, its electrostatic potential V increases proportionally.

$$Q = C V$$

$$C = Q / V$$

$$V = Q / C$$

C = constant of proportionality = Electrical Capacitance

Ability of a conductor/system to store electric charge and electrostatic energy per unit potential increase.

UNITS + DIMENSIONAL FORMULA

- SI unit: Farad (F) = 1 Coulomb / Volt = 1 C/V
- $1 \mu\text{F} = 10^{-6} \text{ F}$
- $1 \text{ nF} = 10^{-9} \text{ F}$
- $1 \text{ pF} = 10^{-12} \text{ F}$
- Dimensional formula: $[M^{-1} L^{-2} T^4 A^2]$

MEMORY LINK: $Q \rightarrow C \rightarrow V$




HOT TOPIC: WHY 1 FARAD IS EXTRAORDINARILY LARGE?

For a spherical conductor: $C = 4\pi \epsilon_0 R$. To have $C = 1 \text{ F}$, the source calculates $R = 9 \times 10^9 \text{ m} = 9,000,000 \text{ km}$. Earth's radius is only $6,400 \text{ km} = 6.4 \times 10^6 \text{ m}$, so a 1-F spherical conductor would be about 1,400 times larger than Earth. Hence practical capacitors use μF or pF .

2. CAPACITANCE OF AN ISOLATED SPHERICAL CONDUCTOR

DERIVATION

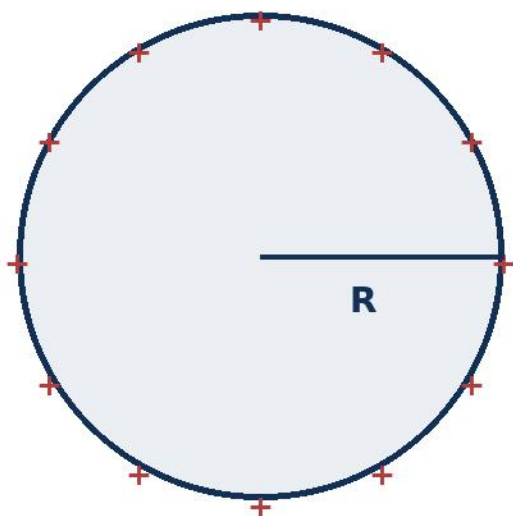

Isolated sphere of radius R carrying total charge Q

Step 1 — Potential at surface:

$$V = (1 / 4\pi \epsilon_0) (Q / R)$$

Step 2 — Apply $C = Q/V$:

$$C = Q / [(1 / 4\pi \epsilon_0)(Q/R)]$$

$$C = 4\pi \epsilon_0 R$$

$$C = 4\pi \epsilon_0 R$$

EFFECT OF MEDIUM

If the sphere is placed in a medium of dielectric constant K (relative permittivity ϵ_r):

$$C_{\text{medium}} = K C_{\text{vacuum}}$$

$$= 4\pi \epsilon_0 K R$$

CBSE BOARD EXAMPLE 2.1 — EARTH CAPACITANCE


Question: Assuming Earth to be a spherical conductor of radius 6,400 km, calculate its capacitance in microfarads (μF).

- $R = 6,400 \text{ km} = 6.4 \times 10^6 \text{ m}$
- $1/(4\pi \epsilon_0) = 9 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$, hence $4\pi \epsilon_0 = 1/(9 \times 10^9) \text{ F/m}$
- Formula: $C = 4\pi \epsilon_0 R$
- Substitute: $C = (1/9 \times 10^9)(6.4 \times 10^6)$
- $C = 6.4/9000 = 0.0007111 \text{ F}$
- Convert: $C = 0.0007111 \times 10^6 \mu\text{F}$

$$\text{FINAL: } C_{\text{Earth}} = 711.1 \mu\text{F}$$

3. PARALLEL PLATE CAPACITOR — COMPLETE DERIVATION

SETUP + DIAGRAM

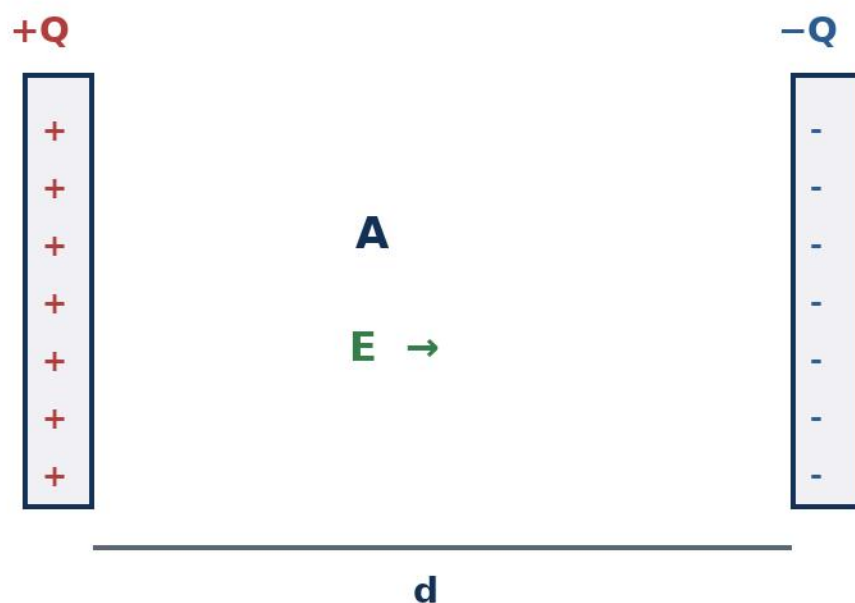

Two parallel conducting plates P_1 and P_2 , each of area A , separated by d in vacuum. P_1 carries $+Q$ and P_2 carries $-Q$; surface charge densities are $+\sigma$ and $-\sigma$.

$$\sigma = Q/A$$

STEP-BY-STEP DERIVATION

1. Electric field between plates

$$E = \sigma/\epsilon_0 = Q/(A \epsilon_0)$$

In the region between oppositely charged plates, the electric fields add up.

2. Potential difference between plates

$$V = Ed = [Q/(A \epsilon_0)] d$$

3. Capacitance

$$C_0 = Q/V = \epsilon_0 A/d$$

RESULT + INTERPRETATION

$$C_0 = \epsilon_0 A/d$$

- Capacitance increases with plate area A .
- Capacitance decreases when separation d increases.
- $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$.

PRINCIPLE OF A CAPACITOR

Bringing an earthed neutral conductor near a charged conductor induces opposite charge on the inner side, lowers the potential of the charged plate, and allows it to hold more charge at the same potential.

4. DIELECTRIC SLAB — POLARIZATION + PARTIAL INSERTION

WHAT A DIELECTRIC DOES



Net field decreases: $E = E_0/K$


CASE A — DIELECTRIC SLAB OF THICKNESS $t < d$

Electric field in air region ($d - t$): E_0

Electric field inside dielectric slab t : $E = E_0/K$

$$V = E_0(d - t) + (E_0/K)t$$

$$= E_0 [d - t(1 - 1/K)]$$

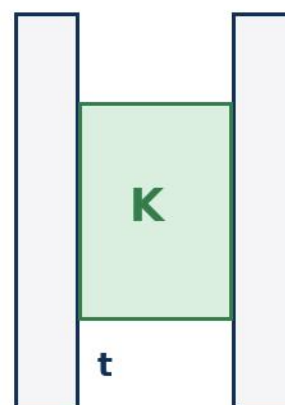

$$C = \epsilon_0 A / [d - t(1 - 1/K)]$$

SPECIAL CASES + CONDUCTING SLAB

$$t = d \rightarrow C = K C_0 = K \epsilon_0 A / d$$

$$\text{Conducting slab: } C = \epsilon_0 A / (d - t)$$

For a conductor, $K \rightarrow \infty$ and $E = 0$ inside. The effective separation becomes $d - t$.

DIELECTRIC vs CONDUCTOR

DIELECTRIC

- E inside = E_0/K
- K is finite
- Partial slab uses $d - t(1 - 1/K)$

CONDUCTOR

- E inside = 0
- $K \rightarrow \infty$
- Effective thickness = $d - t$

5. BATTERY CONNECTED vs DISCONNECTED

BATTERY CONNECTED

$$V = V_0 \text{ (CONSTANT)}$$

Capacitance (C)

Increases: $C = K C_0$

Potential difference (V)

Remains constant: $V = V_0$

Charge (Q)

Increases: $Q = K Q_0$

Electric field (E)

Remains constant: $E = E_0$

Stored energy (U)

Increases: $U = K U_0$

BATTERY DISCONNECTED

$$Q = Q_0 \text{ (CONSTANT)}$$

Capacitance (C)

Increases: $C = K C_0$

Potential difference (V)

Decreases: $V = V_0/K$

Charge (Q)

Remains constant: $Q = Q_0$

Electric field (E)

Decreases: $E = E_0/K$

Stored energy (U)

Decreases: $U = U_0/K$

MEMORY TRICK: BATTERY CONNECTED → V is BOSS | DISCONNECTED → Q is BOSS

6. CAPACITORS IN SERIES & PARALLEL

SERIES COMBINATION



Same charge Q on every capacitor

$$V = V_1 + V_2 + V_3 + \dots$$

$$1/C_s = 1/C_1 + 1/C_2 + 1/C_3 + \dots$$

$$C_s = C_1 C_2 / (C_1 + C_2)$$

VOLTAGE DIVISION

$$V_1 = [C_2 / (C_1 + C_2)] V$$

$$V_2 = [C_1 / (C_1 + C_2)] V$$

Smaller capacitance gets larger voltage in series.


IDENTICAL CAPACITORS

$$C_s = C/n$$

For n identical capacitors of capacitance C :

$$C_p/C_s = n^2$$

PARALLEL COMBINATION

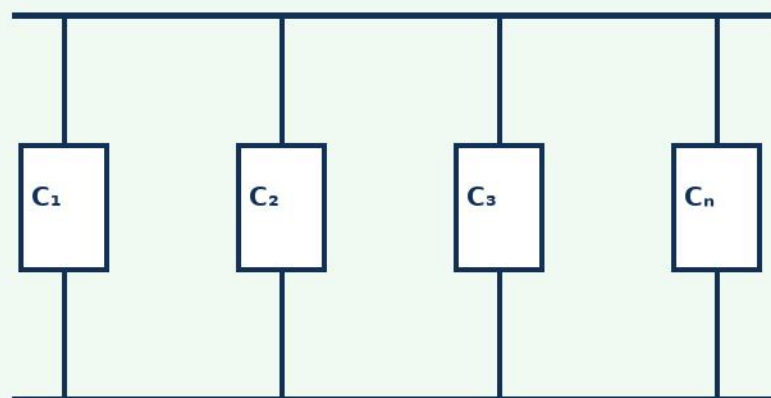

Same voltage V across every capacitor

$$Q = Q_1 + Q_2 + Q_3 + \dots$$

$$C_p = C_1 + C_2 + C_3 + \dots + C_n$$

$$C_p = nC \text{ (identical capacitors)}$$

SERIES vs PARALLEL — AT A GLANCE

Charge	Same	Different
Voltage	Different	Same
Equivalent C	Smaller	Larger
Rule	Add reciprocals	Add directly

7. ENERGY STORED IN A CAPACITOR

PHYSICAL MEANING + DERIVATION

Charging a capacitor transfers charge from one plate to another against electrostatic repulsion. The work done is stored as electrostatic potential energy in the electric field.

Let q be the intermediate charge at potential $v = q/C$.

$$dW = v dq = (q/C) dq$$

$$W = \int_0^Q (q/C) dq = Q^2/(2C)$$

$$U = \frac{1}{2} CV^2 = Q^2/(2C) = \frac{1}{2} QV$$

ENERGY DENSITY

Energy density = energy stored per unit volume between the plates.

$$u = \frac{1}{2} \epsilon_0 E^2$$

SI unit: J/m³

CHARGE-SHARING: COMMON POTENTIAL

$$V_{\text{common}} = (C_1 V_1 + C_2 V_2)/(C_1 + C_2)$$

When two charged capacitors are connected in parallel, charges redistribute until a common potential is reached.

ENERGY LOSS ON SHARING CHARGES

$$\Delta U = C_1 C_2 (V_1 - V_2)^2 / [2(C_1 + C_2)]$$

The loss of electrostatic energy is dissipated as heat and sparks. It is always positive because $(V_1 - V_2)^2 > 0$.

8. CHARGING & DISCHARGING — RC CONCEPTS


TIME CONSTANT

$$\tau = RC$$

SI unit: seconds. τ represents the time taken for charge to reach 63.2% of maximum during charging, or drop to 36.8% during discharging.


CHARGING

$$q(t) = Q_0(1 - e^{-t/RC})$$

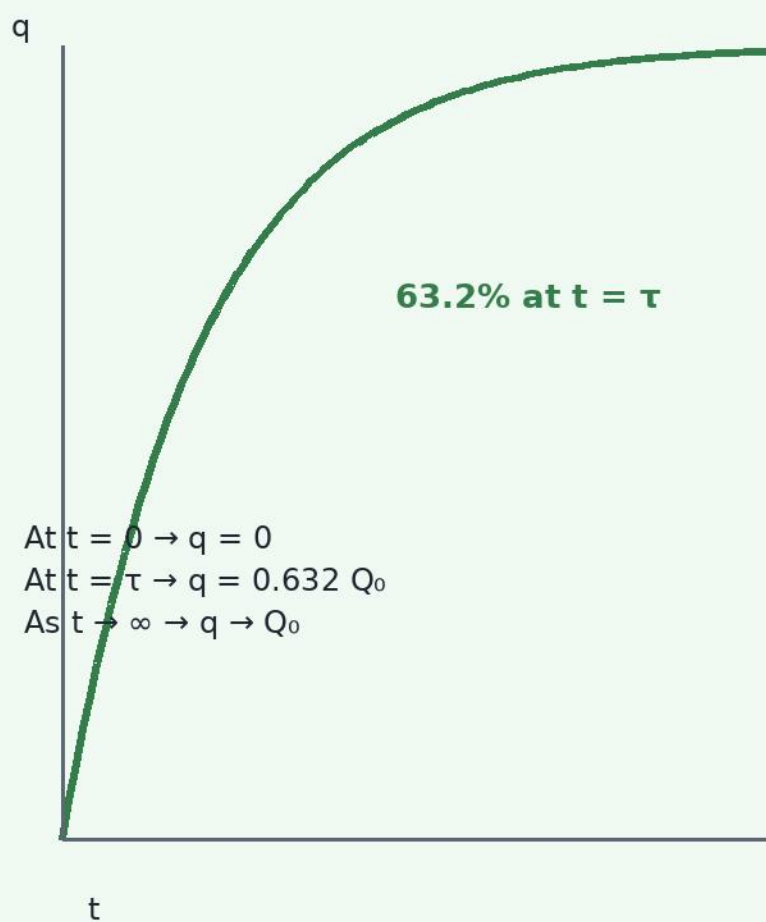

DISCHARGING

$$q(t) = Q_0 e^{-t/RC}$$

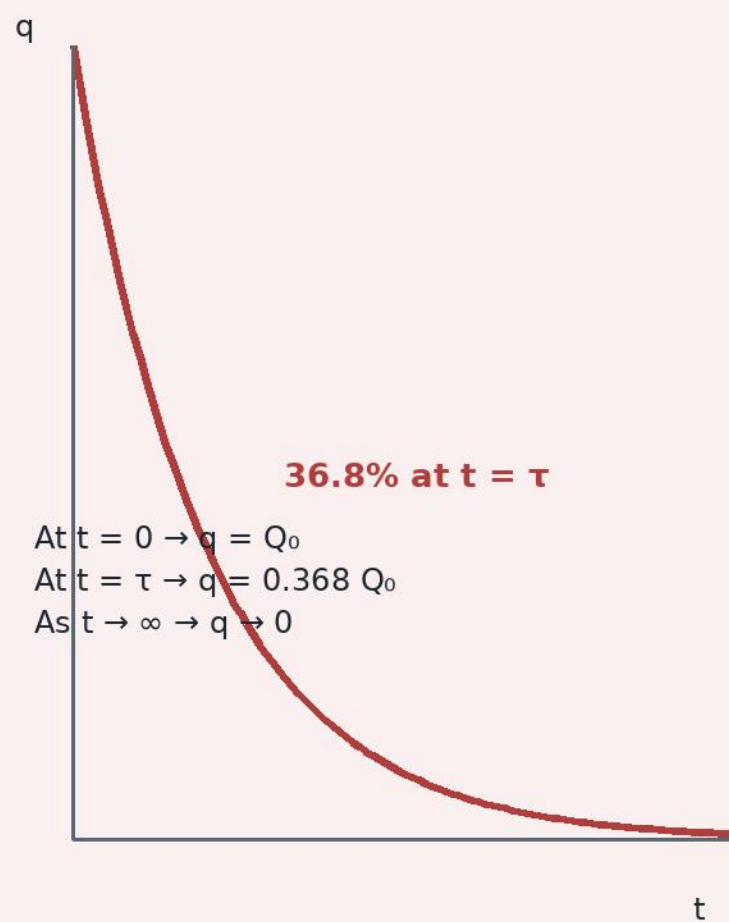

9. CBSE PYQ ZONE — ONLY QUESTIONS PRESENT IN SOURCE

PYQ 1 — CBSE 2024, 3 Marks

QUESTION

A parallel plate capacitor of capacitance C is charged to potential V by a battery. The battery is disconnected and a dielectric slab of $K = 4$ is inserted. Find the ratio of new energy stored to initial energy stored.

$$U_0 = \frac{1}{2}CV^2 = Q^2/(2C)$$

Battery disconnected $\rightarrow Q$ constant

$$C' = 4C$$

$$U' = Q^2/(2C') = U_0/4$$

$$\text{FINAL RATIO: } U'/U_0 = 1:4$$

PYQ 2 — CBSE 2023, 2 Marks

QUESTION

Two capacitors $C_1 = 3 \mu\text{F}$ and $C_2 = 6 \mu\text{F}$ are connected in series across a 12 V battery. Calculate the voltage across the $3 \mu\text{F}$ capacitor.

$$C_s = (3 \times 6)/(3 + 6) = 2 \mu\text{F}$$

$$Q = C_s V = 24 \mu\text{C}$$

Series $\rightarrow$ same Q

$$V_1 = Q/C_1 = 24/3 = 8 \text{ V}$$

$$\text{FINAL: } 8 \text{ V}$$

PYQ 3 — CBSE 2022, 3 Marks

QUESTION

Derive an expression for the capacitance of a parallel plate capacitor filled partially with a dielectric slab of thickness $t < d$.

Use the Case A derivation from Page 4:

$$C = \epsilon_0 A / [d - t(1 - 1/K)]$$

PYQ 4 — CBSE 2020, 3 Marks

QUESTION

Two capacitors $C_1 = 2 \mu\text{F}$ and $C_2 = 4 \mu\text{F}$ charged to $V_1 = 100 \text{ V}$ and $V_2 = 50 \text{ V}$ respectively are connected in parallel. Find common potential and energy loss.

$$V_{\text{common}} = [(2 \times 100) + (4 \times 50)]/(2 + 4) = 66.67 \text{ V}$$

$$\Delta U = C_1 C_2 (V_1 - V_2)^2 / [2(C_1 + C_2)]$$

$$= 1.67 \times 10^{-3} \text{ J}$$

10. COMMON EXAM MISTAKES — DON'T LOSE EASY MARKS

Forgetting unit conversions

- ❑ Wrong: substitute μF or pF directly in calculations requiring F .
- ❑ Correct: $\mu\text{F} \rightarrow 10^{-6} \text{ F}$; $\text{pF} \rightarrow 10^{-12} \text{ F}$ before energy/charge equations.

Confusing series / parallel formulas

- ❑ Wrong: swap capacitor series formula with resistor parallel formula.
- ❑ Correct: Series $\rightarrow$ add reciprocals; Parallel $\rightarrow$ add directly.

Misapplying battery condition

- ❑ Wrong: treat V and Q as constant simultaneously.
- ❑ Correct: Battery connected $\rightarrow V$ constant. Disconnected $\rightarrow Q$ constant.

Neglecting dielectric slab thickness

- ❑ Wrong: use $K\epsilon_0 A/d$ for a partial slab.
- ❑ Correct: $C = \epsilon_0 A/[d - t(1 - 1/K)]$ when $t < d$.

GOLDEN CHECK BEFORE YOU SOLVE

- 1) Convert units
- 2) Identify connected/disconnected
- 3) Decide series/parallel
- 4) Check dielectric thickness
- 5) Write the final unit.

11. PRACTICE ZONE — BOARD PATTERN

BASIC

$$C = Q/V$$

$$Q = CV$$

$$V = Q/C$$

SPHERE

$$C = 4\pi \epsilon_0 R$$

PARALLEL PLATE

$$C_0 = \epsilon_0 A/d$$

DIELECTRIC

$$C = K C_0 = K \epsilon_0 A/d$$

PARTIAL SLAB

$$C = \epsilon_0 A/[d - t(1 - 1/K)]$$

CONDUCTING SLAB

$$C = \epsilon_0 A/(d - t)$$

SERIES

$$1/C_s = 1/C_1 + 1/C_2 + \dots$$

$$Q \text{ is same}$$

TWO IN SERIES

$$C_s = C_1 C_2 / (C_1 + C_2)$$

PARALLEL

$$C_p = C_1 + C_2 + \dots$$

$$V \text{ is same}$$

IDENTICAL

$$C_s = C/n$$

$$C_p = nC$$

$$C_p/C_s = n^2$$

ENERGY

$$U = \frac{1}{2} CV^2$$

$$U = Q^2/(2C)$$

$$U = \frac{1}{2} QV$$

ENERGY DENSITY

$$u = \frac{1}{2} \epsilon_0 E^2$$

$$\text{SI: J/m}^3$$

CHARGE SHARING

$$V_{\text{common}} = (C_1 V_1 + C_2 V_2) / (C_1 + C_2)$$

ENERGY LOSS

$$\Delta U = C_1 C_2 (V_1 - V_2)^2 / [2(C_1 + C_2)]$$

TIME CONSTANT

$$\tau = RC$$

$$\text{SI: seconds}$$

CHARGING

$$q(t) = Q_0 (1 - e^{-t/RC})$$

$$63.2\% \text{ at } \tau$$

DISCHARGING

$$q(t) = Q_0 e^{-t/RC}$$

$$36.8\% \text{ at } \tau$$

MEMORY MAP

ELECTRICAL CAPACITANCE → Definition → Sphere → Parallel Plate → Dielectric → Battery Cases → Series/Parallel → Energy → RC →